

Practical No.01: Ripple Carry Adder

entity OR_gate is

Port (p : in STD_LOGIC;

q : in STD_LOGIC;

r : out STD_LOGIC);

end OR_gate;

architecture Behavioral of OR_gate is

begin

r<= p or q;

end Behavioral;

entity Half_adder is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

s : out STD_LOGIC;

c : out STD_LOGIC);

end Half_adder;

architecture Behavioral of Half_adder is

begin

s<= a xor b;

c<= a and b;

end Behavioral;

entity Full_adder is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

Cin : in STD_LOGIC;

Sum : out STD_LOGIC;

Cout : out STD_LOGIC);

end Full_adder;

architecture struct of Full_adder is

Component Half_adder is

Port (a : in STD_LOGIC;

b : in STD_LOGIC;

s : out STD_LOGIC;

c : out STD_LOGIC);

end component;

Component OR_gate is

Port (p : in STD_LOGIC;

q : in STD_LOGIC;

r : out STD_LOGIC);

end component;

```
signal temp1,temp2,temp3 : std_logic;
```

```
begin
```

```
U1: Half_adder port map(A,B,temp1,temp2);
```

```
U2: Half_adder port map(temp1,Cin,Sum,temp3);
```

```
U3: OR_gate port map(temp2,temp3,Cout);
```

```
end struct;
```

With Ripple carry adder

entity RCA is

```
Port ( X : in STD_LOGIC_VECTOR (3 downto 0);
```

```
Y : in STD_LOGIC_VECTOR (3 downto 0);
```

```
Zin : in STD_LOGIC;
```

```
RCASum : out STD_LOGIC_VECTOR (3 downto 0);
```

```
RCACout : out STD_LOGIC);
```

```
end RCA;
```

architecture Behavioral of RCA is

component Full_adder is

```
Port ( A : in STD_LOGIC;
```

```
B : in STD_LOGIC;
```

```
Cin : in STD_LOGIC;
```

```
Sum : out STD_LOGIC;
```

```
        Cout : out STD_LOGIC);

end component;

signal Carry : std_logic_vector(2 downto 0);

begin

u1: Full_adder port map(X(0),Y(0),Zin,RCASum(0),Carry(0));
u2: Full_adder port map(X(1),Y(1),Carry(0),RCASum(1),Carry(1));
u3: Full_adder port map(X(2),Y(2),Carry(1),RCASum(2),Carry(2));
u4: Full_adder port map(X(3),Y(3),Carry(2),RCASum(3),RCACout);

end Behavioral;
```

Practical No.02: Arithmetic Logic Unit

★ CODE:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_unsigned.ALL;

entity ALU is
  Port (
    A : in STD_LOGIC_VECTOR (3 downto 0);
    B : in STD_LOGIC_VECTOR (3 downto 0);
    Cin : in STD_LOGIC;
    Sel : in STD_LOGIC_VECTOR (3 downto 0);
    Y : out STD_LOGIC_VECTOR (3 downto 0));
end ALU;
architecture concurrent of ALU is
begin
  Y<= A when Sel = "0000" else
    A+1 when Sel = "0001" else
    B when Sel = "0010" else
    B+1 when Sel = "0011" else
    A+B when Sel = "0100" else
    A+B+Cin when Sel = "0101" else
    A-B when Sel = "0110" else
    B-1 when Sel = "0111" else
    A or B when Sel = "1000" else
    A nor B when Sel = "1001" else
    A nand B when Sel = "1010" else
    A and B when Sel = "1011" else
    not(A) when Sel = "1100" else
    A xor B when Sel = "1101" else
    A xnor B when Sel = "1110" else
    not(B) ;
end concurrent;
```

★ Test Bench CODE:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_unsigned.ALL;


entity ALU_tb is
  -- Port ( );
end ALU_tb;
architecture Behavioral of ALU_tb is
  component ALU is
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
```

```

    B : in STD_LOGIC_VECTOR (3 downto 0);
    Cin : in STD_LOGIC;
    Sel : in STD_LOGIC_VECTOR (3 downto 0);
    Y : out STD_LOGIC_VECTOR (3 downto 0));
end component;
signal A, B, Y : std_logic_vector (3 downto 0);
signal Cin : std_logic;
signal Sel : std_logic_vector(3 downto 0) := "0000";
begin
u1: ALU port map (A, B, Cin, Sel, Y);
process
begin
    A <= "1010";
    B <= "1111";
    Cin <= '0';
    Sel <= Sel + 1;
    wait for 100 ns;
    Cin <= '1';
    wait for 100 ns;
end process;
end Behavioral;

```

→ **OUTPUT:**

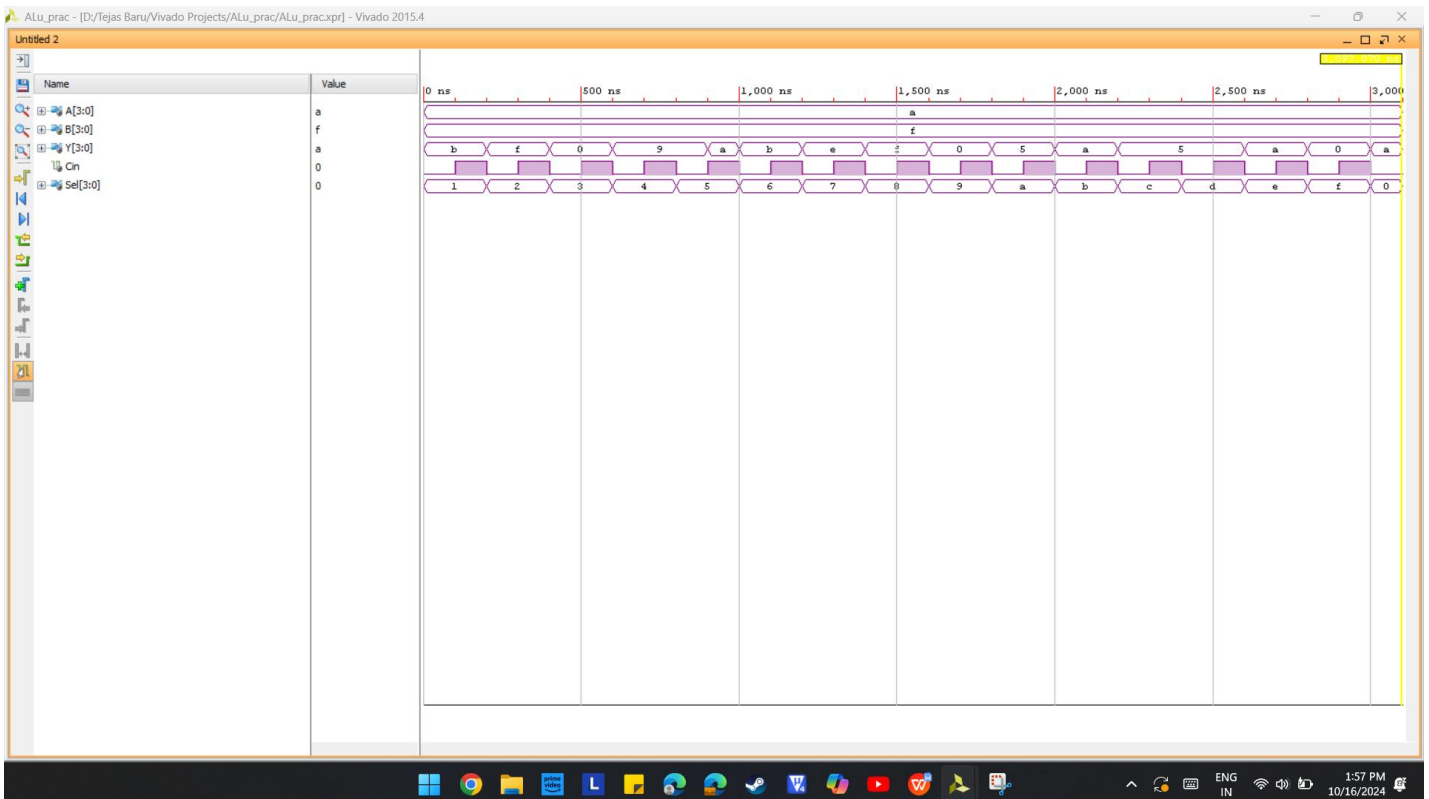

Practical No.03: Universal Shift Register

★ CODE:

```
Use library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.NUMERIC_STD.ALL;

entity usr1 is
  Port (
    clk : in  STD_LOGIC;
    clk_div : inout std_logic;
    rst : in  STD_LOGIC;
    load: in  STD_LOGIC;
    mode : in  STD_LOGIC_VECTOR(1 downto 0); -- mode selection input
    si : in  STD_LOGIC; -- serial input
    pi : in  STD_LOGIC_VECTOR(3 downto 0); -- parallel input
    so : out STD_LOGIC; -- serial output
    po : out STD_LOGIC_VECTOR(3 downto 0) -- parallel output
  );
end usr1;
architecture Behavioral of usr1 is
  signal shift_reg : STD_LOGIC_VECTOR(3 downto 0);
  signal counter: std_logic_vector(26 downto 0):=( others=>'0');
begin
  process(clk_div, rst,load)
  begin
    if rst = '1' then
      shift_reg <= (others => '0');
    elsif clk_div'event and clk_div= '1' then
      case mode is
        when "00" => -- SISO mode
          shift_reg( 3 downto 1) <= shift_reg(2 downto 0);
          shift_reg(0)<=si;
          so <= shift_reg(3);
        when "01" => -- SIPO mode
          shift_reg( 3 downto 1) <= shift_reg(2 downto 0);
          shift_reg(0)<=si;
          po <= shift_reg;
        when "10" => -- PISO mode
          if(load='0') then
            shift_reg <= pi;
          else
            shift_reg( 3 downto 1) <= shift_reg(2 downto 0);
          end if;
          so <= shift_reg(3);
        when "11" => -- PIPO mode
```

```

        po<= pi;
        when others =>
            null;
        end case;
    end if;
end process;
-- so <= shift_reg(3);
-- po <= shift_reg;
process(clk)
begin
    if clk'event and clk = '1' then
        if rst = '1' then
            counter <= (others => '0');
        else
            counter <= counter + '1';
        end if;
    end if;
end process;
clk_div<= counter(0);
end Behavioral;

```

★ Test Bench CODE:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity usr1tb is
end usr1tb;
architecture Behavioral of usr1tb is
    signal clk,clk_div : STD_LOGIC := '0';
    signal rst : STD_LOGIC := '0';
    signal load : STD_LOGIC := '0';
    signal mode : STD_LOGIC_VECTOR(1 downto 0) := "00";
    signal si : STD_LOGIC := '0';
    signal pi : STD_LOGIC_VECTOR(3 downto 0) := (others => '0');
    signal so : STD_LOGIC;
    signal po : STD_LOGIC_VECTOR(3 downto 0);
    component usr1
        Port (
            clk : in  STD_LOGIC;
            clk_div : inout std_logic;
            rst : in  STD_LOGIC;
            load: in  STD_LOGIC;
            mode : in  STD_LOGIC_VECTOR(1 downto 0);
            si : in  STD_LOGIC;
            pi : in  STD_LOGIC_VECTOR(3 downto 0);

```



```

        so : out STD_LOGIC;
        po : out STD_LOGIC_VECTOR(3 downto 0)
    );
end component;
begin
    uut : usr1
        Port Map (
            clk => clk,
            clk_div => clk_div,
            rst => rst,
            load => load,
            mode => mode,
            si => si,
            pi => pi,
            so => so,
            po => po
        );
    clk_process : process
    begin
        clk <= '0';
        wait for 10 ns;
        clk <= '1';
        wait for 10 ns;
    end process;
    stim_proc : process
    begin
        -- Reset the UUT
        rst <= '1';
        wait for 20 ns;
        rst <= '0';
        -- Test SISO mode
        mode <= "00";
        si <= '1';
        wait for 200 ns;
        si <= '0';
        wait for 200 ns;
        -- Test SIPO mode
        mode <= "01";
        si <= '1';
        wait for 100 ns;
        si <= '0';
        wait for 200 ns;
        -- Test PISO mode
        mode <= "10";
        load <= '0';
        pi <= "1110";
        wait for 100 ns;
        load <= '1';
    end process;
end


```

```

wait for 300 ns;
-- Test PIPO mode
mode <= "11";
pi <= "1010";
wait for 50 ns;
pi <= "1100";
wait for 50 ns;
wait;
end process;
end Behavioral;

```

→ **OUTPUT:**

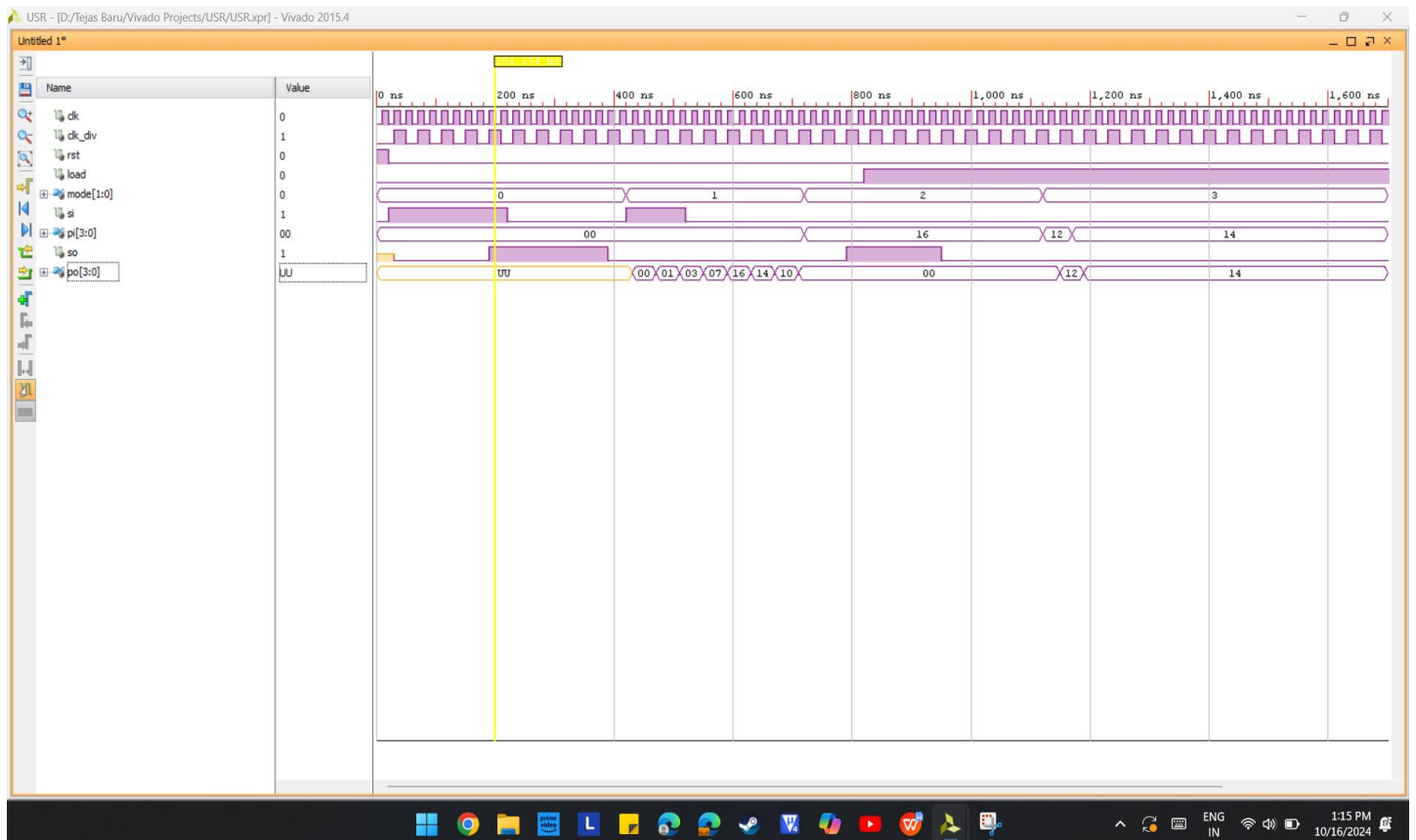

Practical No.04: MOD-N Counter

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity count is
    Port ( clk : in STD_LOGIC;
          clk_div: inout std_logic;
          rst : in STD_LOGIC;
          an    : out std_logic_vector(3 downto 0);
          seg   : out std_logic_vector(6 downto 0);
          q : inout STD_LOGIC_VECTOR (3 downto 0));
end count;

architecture Behavioral of count is
    signal count : std_logic_vector( 25 downto 0):= (others => '0');

begin
    an<="0001";
    process(clk_div,rst)
        variable temp: std_logic_vector(3 downto 0):="0000";
    begin
        if (rst='1') then
            temp:= "0000";
        elsif (clk_div'event and clk_div='1') then
            temp:= temp+'1';
            if( temp > "1001") then
                temp := "0000";
            end if;
        end if;
```

```

end if;
q<=temp;
end process;
process(clk)
begin
if (clk'event and clk='1') then
count <= count + '1';
end if;
clk_div<= count(25);
end process;
--clk_div<= count(1);
process(q)
begin
case q is
    when "0000" => seg <= "1000000"; -- 0
    when "0001" => seg <= "1001111"; -- 1
    when "0010" => seg <= "0100100"; -- 2
    when "0011" => seg <= "0110000"; -- 3
    when "0100" => seg <= "0011001"; -- 4
    when "0101" => seg <= "0010010"; -- 5
    when "0110" => seg <= "0000010"; -- 6
    when "0111" => seg <= "1111000"; -- 7
    when "1000" => seg <= "0000000"; -- 8
    when "1001" => seg <= "0010000"; -- 9
    when others => seg <= "1111111";
end case;
end process;
end Behavioral;

```

Testbench for Counter :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity COUNTER_TB is
-- Port ( );
end COUNTER_TB;

architecture Behavioral of COUNTER_TB is
COMPONENT count is
    Port ( clk : in STD_LOGIC;
          clk_div: inout std_logic;
          rst : in STD_LOGIC;
          q : inout STD_LOGIC_VECTOR (3 downto 0));
end component;

signal clk,clk_div: std_logic;
signal rst:std_logic;
signal q: std_logic_vector(3 downto 0);

begin


u1: count port map(clk,clk_div,rst,q);

process
begin
    clk<='1';
    wait for 100 ns;
    clk<='0';
    wait for 100 ns;
end process;

rst<='1', '0' after 300 ns ;
```

end Behavioral;

Counter O/P:

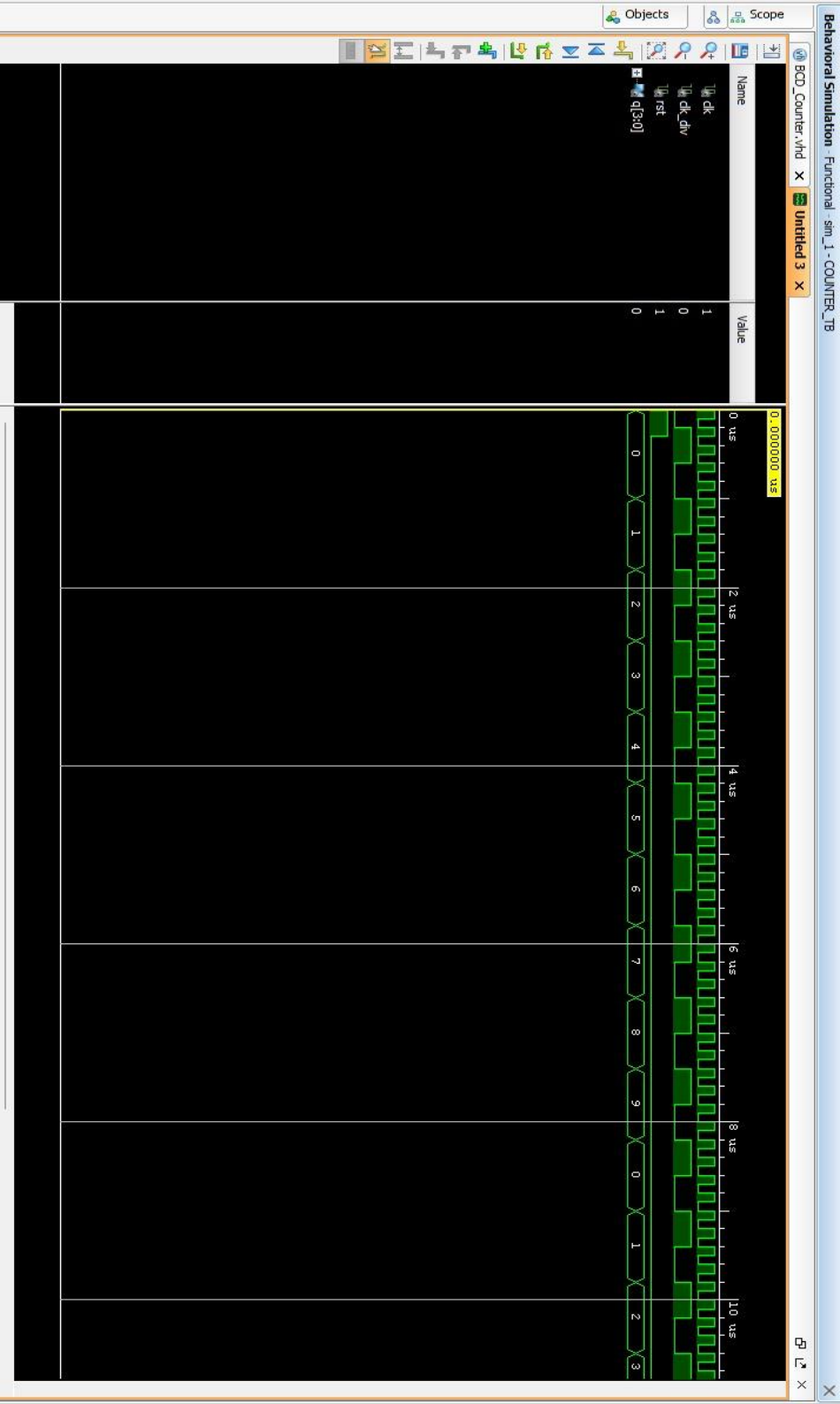

Practical No.05: FIFO :

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity fifo_correct is
  GENERIC
  (
    ADDRESS_WIDTH : integer:=2;---8 bit
    DATA_WIDTH : integer:=4 ---32 bit
  );
  port ( clk : in std_logic;
        clk_div : inout std_logic;
        reset : in std_logic;
        enr : in std_logic; --enable read,should be '0' when not in use.
        enw : in std_logic; --enable write,should be '0' when not in use.
        dataout : out std_logic_vector(DATA_WIDTH-1 downto 0); --output data
        datain : in std_logic_vector (DATA_WIDTH-1 downto 0); --input data
        empty : out std_logic; --set as '1' when the queue is empty
        err : out std_logic;
        full : out std_logic --set as '1' when the queue is full
  );
end fifo_correct;

architecture Behavioral of fifo_correct is
```

```
type memory_type is array (0 to ((2**ADDRESS_WIDTH)-1)) of
std_logic_vector(DATA_WIDTH-1 downto 0);
```

```
-----distributed-----
```

```
signal memory : memory_type ;-- :=(others => (others => '0')); --memory for
queue.-----
```

```
signal readptr,writeptr : std_logic_vector(ADDRESS_WIDTH-1 downto 0); --read
and write pointers.
```

```
signal full0 : std_logic;
```

```
signal empty0 : std_logic;
```

```
signal counter: std_logic_vector(28 downto 0):=( others=>'0');
```

```
begin
```

```
full <= full0;
```

```
empty <= empty0;
```

```
fifo0: process(clk_div,reset,datain,enw,enr)
```

```
begin
```

```
if reset='1' then
```

```
readptr <= (others => '0');
```

```
writeptr <= (others => '0');
```

```
empty0 <='1';
```

```
full0<='0';
```

```
err<='0';
```

```
elsif clk_div'event and clk_div = '1' then
```

```
if enw='1' and full0='0' then
```

```
memory (conv_integer(writeptr)) <= datain ;
```

```
writeptr <= writeptr + '1' ;
```

```
if (writeptr + '1' = readptr) then
```

```
full0<='1';
```



```

empty0<= '0';
else
full0<='0';
empty0<= '1';
end if ;
end if ;
if enr='1' and empty0='0' then
dataout <= memory (conv_integer(readptr));
readptr <= readptr + '1' ;
    if (readptr + '1' = writeptr ) then
        empty0<='1';
        full0<='0';
    else
        empty0<='0';
        full0<='1';
    end if ;
end if ;
if (empty0='1' and enr='1') or (full0='1' and enw='1') then
err<='1';
else
err<= '0';
end if ;
end if;
end process;

process(clk)

```

```

begin
if clk'event and clk= '1' then
counter<= counter + '1';
end if;
end process;
clk_div<= counter(25);
end Behavioral;

```

Testbench for FIFO :

```

LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

ENTITY fifo_test IS
END fifo_test;

ARCHITECTURE behavior OF fifo_test IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT fifo_correct

    PORT(

        clk : in std_logic;

        clk_div : inout std_logic;

        reset : in std_logic;

        enr : in std_logic; --enable read,should be '0' when not in use.

        enw : in std_logic; --enable write,should be '0' when not in use.

        dataout : out std_logic_vector(3 downto 0); --output data

        datain : in std_logic_vector (3 downto 0); --input data

        empty : out std_logic; --set as '1' when the queue is empty

        err : out std_logic;

        full : out std_logic --set as '1' when the queue is full

```

```

    );
END COMPONENT;

--Inputs
signal clk : std_logic := '0';
signal reset,clk_div: std_logic;
signal enr : std_logic := '0';
signal enw : std_logic := '0';
signal datain : std_logic_vector(3 downto 0) := (others => '0');

--Outputs
signal dataout : std_logic_vector(3 downto 0);
signal empty : std_logic;
signal err : std_logic;
signal full : std_logic;
-- Clock period definitions
constant clk_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: fifo_correct PORT MAP (
        clk => clk,
        clk_div=>clk_div,
        reset=>reset,
        enr => enr,
        enw => enw,
        dataout => dataout,
        datain => datain,
        empty => empty,

```


```

        err => err,
        full => full
    );
-- Clock process definitions
clk_process :process
begin
    clk <= '0';
    wait for clk_period/2;
    clk <= '1';
    wait for clk_period/2;
end process;
reset<='1','0' after 50ns;
enw<= '1', '0' after 200 ns ;
enr<= '0','1' after 200 ns ;
--Stimulus process
stim_proc: process
begin
    datain<="1010";
    wait for 10 ns;
    datain<="1111";
    wait for 10 ns;
    datain<="1001";
wait for 10 ns;
    datain<="0001";
    wait for 10 ns;
end process;

```

END behavior;

FIFO O/P :

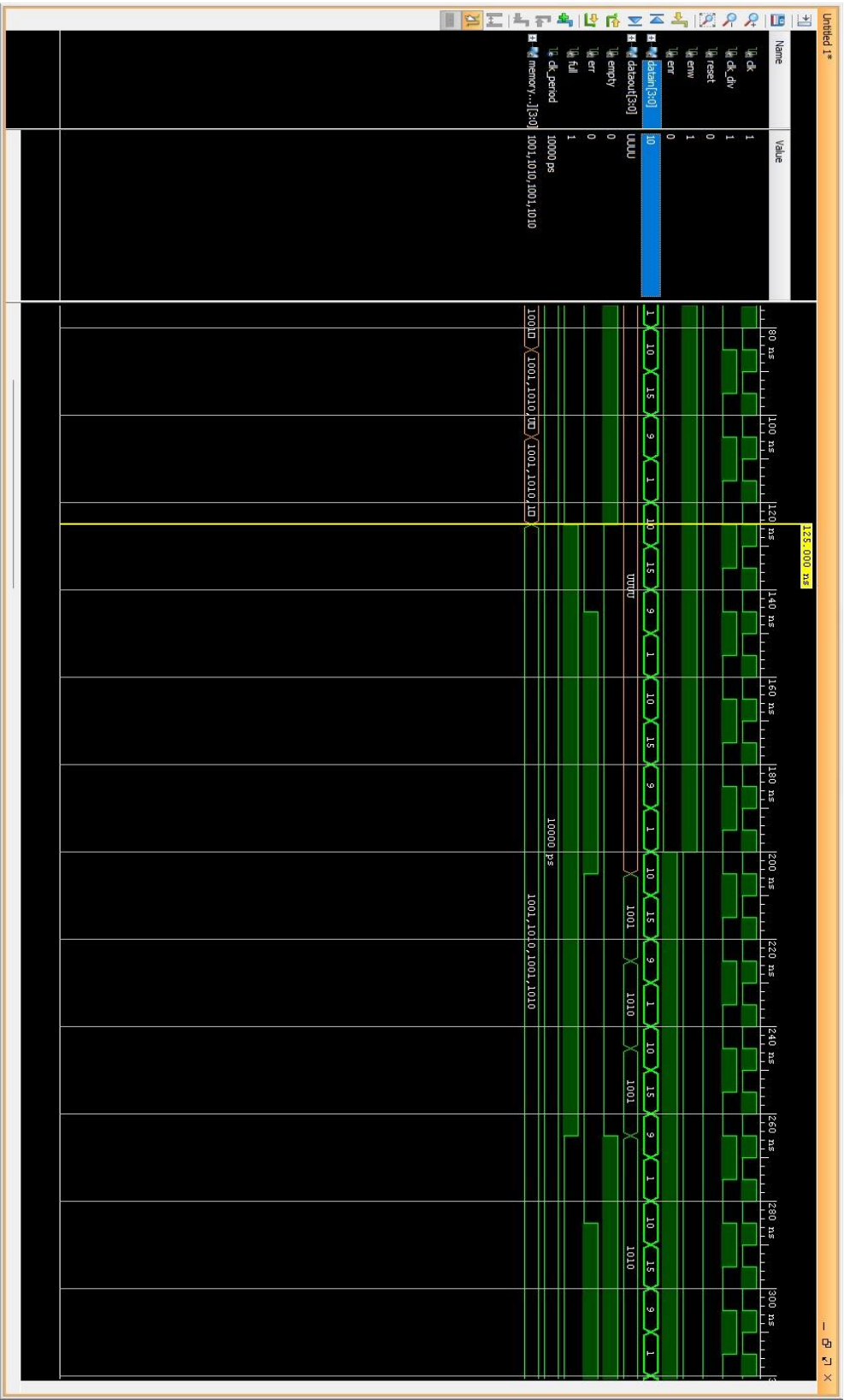

Practical No.06: LCD

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity lcdm is
    Port ( clk : in  STD_LOGIC;
          rst : in  STD_LOGIC;
          lcd_data : out  STD_LOGIC_VECTOR (7 downto 0);
          lcd_rs : out  STD_LOGIC;
          lcd_rw : out  STD_LOGIC;
          lcd_en : out  STD_LOGIC);
end lcdm;

architecture Behavioral of lcdm is
    signal lcd_init : STD_LOGIC := '0';
    signal lcd_data_reg : STD_LOGIC_VECTOR (7 downto 0) := (others => '0');
    signal counter: std_logic_vector(28 downto 0):= (others => '0');
    signal en_pulse : std_logic := '0';
    signal pulse_counter : integer range 0 to 100 := 0; -- 100 clock cycles = 1 us at 100 MHz
    signal state : integer := 0;
    signal clk_enable : STD_LOGIC := '0';
begin
    process(clk)
    begin
        if clk'event and clk = '1' then

            counter <= counter + 1;
            if counter(10) = '1' then
                clk_enable <= '1';
            else
                clk_enable <= '0';
            end if;
        end if;
    end process;

    lcd_data <= lcd_data_reg;

    process(clk_enable)
    begin
        if clk_enable'event and clk_enable = '1' then

            if rst = '1' then
                lcd_init <= '0';
                lcd_data_reg <= (others => '0');
                en_pulse <= '0';
                pulse_counter <= 0;
                state <= 0;
            else
                case state is
                    when 0 =>
                        -- Initialize LCD
```

```

    lcd_data_reg <= "00111000"; -- Function set command
    lcd_rs <= '0';
    lcd_rw <= '0';
    en_pulse <= '1';
    pulse_counter <= 0;
    state <= 1;

when 1 =>
    if pulse_counter < 100 then
        lcd_en <= '1';
        pulse_counter <= pulse_counter + 1;
    else
        lcd_en <= '0';
        en_pulse <= '0';
        pulse_counter <= 0;
        state <= 2; -- Move to next state
    end if;
when 2 =>
    -- Send Display ON command
    lcd_data_reg <= "00001100"; -- Display ON, Cursor OFF
    lcd_rs <= '0';
    lcd_rw <= '0';
    en_pulse <= '1';
    pulse_counter <= 0;
    state <= 3;

when 3 =>
    if pulse_counter < 100 then
        lcd_en <= '1';
        pulse_counter <= pulse_counter + 1;
    else
        lcd_en <= '0';
        en_pulse <= '0';
        pulse_counter <= 0;
        state <= 4;
    end if;
when 4 =>
    -- Send Clear Display command
    lcd_data_reg <= "00000001";
    lcd_rs <= '0';
    lcd_rw <= '0';
    en_pulse <= '1';
    pulse_counter <= 0;
    state <= 5;

when 5 =>
    if pulse_counter < 100 then
        lcd_en <= '1';
        pulse_counter <= pulse_counter + 1;
    else
        lcd_en <= '0';
        en_pulse <= '0';
        pulse_counter <= 0;
        state <= 6;
    end if;
when 6 =>
    -- Send H

```

```

    lcd_data_reg <= "01001000"; -- 'H'
    lcd_rs <= '1';
    lcd_rw <= '0';
    en_pulse <= '1';
    pulse_counter <= 0;
    state <= 7;

when 7 =>
    if pulse_counter < 100 then
        lcd_en <= '1';
        pulse_counter <= pulse_counter + 1;
    else
        lcd_en <= '0';
        en_pulse <= '0';
        pulse_counter <= 0;
        state <= 8;
    end if;
when 8 =>
    -- Send 'e'
    lcd_data_reg <= "01000101"; -- 'E'
    lcd_rs <= '1';
    lcd_rw <= '0';
    en_pulse <= '1';
    pulse_counter <= 0;
    state <= 9;
when 9 =>
    if pulse_counter < 100 then
        lcd_en <= '1';
        pulse_counter <= pulse_counter + 1;
    else
        lcd_en <= '0';
        en_pulse <= '0';
        pulse_counter <= 0;
        state <= 10;
    end if;
when 10 =>
    -- Send 'l'
    lcd_data_reg <= "01001100"; -- 'L'
    lcd_rs <= '1';
    lcd_rw <= '0';
    en_pulse <= '1';
    pulse_counter <= 0;
    state <= 11;
when 11 =>
    if pulse_counter < 100 then
        lcd_en <= '1';
        pulse_counter <= pulse_counter + 1;
    else
        lcd_en <= '0';
        en_pulse <= '0';
        pulse_counter <= 0;
        state <= 12;
    end if;
when 12 =>
    -- Send 'L'
    lcd_data_reg <= "01001100"; -- 'L'
    lcd_rs <= '1';


```



```

        lcd_rw <= '0';
        en_pulse <= '1';
        pulse_counter <= 0;
        state <= 13;
    when 13 =>
        if pulse_counter < 100 then
            lcd_en <= '1';
            pulse_counter <= pulse_counter + 1;
        else
            lcd_en <= '0';
            en_pulse <= '0';
            pulse_counter <= 0;
            state <= 14;
        end if;
    when 14 =>
        -- Send 'o'
        lcd_data_reg <= "01001111"; -- 'O'
        lcd_rs <= '1';
        lcd_rw <= '0';
        en_pulse <= '1';
        pulse_counter <= 0;
        state <= 15;
    when 15 =>
        if pulse_counter < 100 then
            lcd_en <= '1';
            pulse_counter <= pulse_counter + 1;
        else
            lcd_en <= '0';
            en_pulse <= '0';
            pulse_counter <= 0;
            state <= 0; -- Stay in this state
        end if;
    when others =>
        lcd_data_reg <= (others => '0');
        lcd_rs <= '0';
        lcd_rw <= '0';
        en_pulse <= '0';
    end case;
end if;
end if;
end process;

```

 

end Behavioral;